



EEF-205E

Introduction to Logic Design

HW3

Mehmet Ünlü-040230253

Part I

x	y	z	A	B	C	M
0	0	0	1	0	0	1
0	0	1	2	0	1	0
0	1	0	3	0	1	0
0	1	1	4	1	0	0
1	0	0	2	0	1	0
1	0	1	3	0	1	1
1	1	0	4	1	0	0
1	1	1	5	1	0	1

$$A = \sum_m (3, 6, 7)$$

$$B = \sum_m (1, 2, 4, 5)$$

$$C = \sum_m (0, 2, 5, 7)$$

$$M = \sum_m (3, 5, 6, 7)$$

x\y	00	01	11	10
0			1	
1		1	1	1

$$A = xy + yz$$

x\y	00	01	11	10
0		1		1
1	1			1

$$B = xy' + y'z + x'yz'$$


x\y	00	01	11	10
0	1			1
1		1	1	

$$C = y'z' + yz$$


x\y	00	01	11	10
0			1	
1		1	1	1

$$M = xy + xz + yz$$


$$A = xy + u_2$$

 

$$B = xy' + y'z + x'y z'$$

 


$$C = y'z' + yz$$

 


BAYKAR

$$M = xy + y$$

 

$$M = xy + yz + xz$$

 

Part 2

HA

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity HALF_ADDER is
```

```
    Port ( A : in  STD_LOGIC;
```

```
          B : in  STD_LOGIC;
```

```
          S : out STD_LOGIC;
```

```
          Cout : out STD_LOGIC);
```

```
end HALF_ADDER;
```

```
architecture Dataflow of HALF_ADDER is
```


```
begin
```

```
    -- Dataflow Modeling
```

```
    S <= A xor B;
```

```
    Cout <= A and B;
```

```
end Dataflow;
```

 

HA Testbench

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

-- Sadece simülasyon amacıyla kullanılır, sentezlenemez.

```
entity HALF_ADDER_TB is
```

```
end HALF_ADDER_TB;
```

```
architecture Behavioral of HALF_ADDER_TB is
```

```
-- Test edilecek bileşenin (HA) tanımlanması  
component HALF_ADDER  
Port ( A : in STD_LOGIC;  
      B : in STD_LOGIC;  
      S : out STD_LOGIC; -- Sum  
      Cout : out STD_LOGIC); -- Carry Out  
end component;  
  
-- Sinyal tanımlamaları (HA'nın giriş/çıkışlarını bağlamak  
için)  
signal A_TB, B_TB : STD_LOGIC := '0'; -- Başlangıçta 0  
atanır  
signal S_TB, Cout_TB : STD_LOGIC;  
  
-- Simülasyon için zaman sabiti  
constant Clock_Period : time := 10 ns;  
  
begin
```


-- Test edilecek bileşenin bağlanması (Instance)

uut: HALF_ADDER

port map (

 A => A_TB,

 B => B_TB,

 S => S_TB,

 Cout => Cout_TB

);

-- Giriş Vektörlerini Üreten İşlem (Stimulus)

stim_proc: process

begin

 -- Başlangıç (A=0, B=0)

 wait for Clock_Period;

 -- Test 1: A=0, B=1

 B_TB <= '1';

 wait for Clock_Period;

-- Test 2: A=1, B=0

A_TB <= '1';

B_TB <= '0';

wait for Clock_Period;

-- Test 3: A=1, B=1

B_TB <= '1';


wait for Clock_Period;

-- Simülasyonu sonlandır

wait;

end process;

end Behavioral;

 

FA

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

entity FULL_ADDER is

Port (A : in STD_LOGIC;

B : in STD_LOGIC;

Cin : in STD_LOGIC; -- Carry In

```
S : out STD_LOGIC; -- Sum
Cout : out STD_LOGIC); -- Carry Out
end FULL_ADDER;
```

architecture Dataflow of FULL_ADDER is

begin

-- Dataflow Modeling


-- Toplam (S) için denklem: $A \oplus B \oplus C_{in}$

$S \leq A \text{ xor } B \text{ xor } C_{in};$

-- Elde (Cout) için sadeleştirilmiş denklem: $(A \text{ AND } B) \text{ OR } (A \text{ AND } C_{in}) \text{ OR } (B \text{ AND } C_{in})$

$Cout \leq (A \text{ and } B) \text{ or } (A \text{ and } C_{in}) \text{ or } (B \text{ and } C_{in});$

end Dataflow;

 

FA Testbench

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

-- Sadece simülasyon amacıyla kullanılır, sentezlenemez.

```
entity HALF_ADDER_TB is
```

```
end HALF_ADDER_TB;
```

```
architecture Behavioral of HALF_ADDER_TB is
```



```
-- Test edilecek bileşenin (HA) tanımlanması  
component HALF_ADDER  
Port ( A : in STD_LOGIC;  
      B : in STD_LOGIC;  
      S : out STD_LOGIC; -- Sum  
      Cout : out STD_LOGIC); -- Carry Out  
end component;  
  
-- Sinyal tanımlamaları (HA'nın giriş/çıkışlarını bağlamak  
için)  
signal A_TB, B_TB : STD_LOGIC := '0'; -- Başlangıçta 0  
atanır  
signal S_TB, Cout_TB : STD_LOGIC;  
  
-- Simülasyon için zaman sabiti  
constant Clock_Period : time := 10 ns;  
  
begin
```

-- Test edilecek bileşenin bağlanması (Instance)

uut: HALF_ADDER

port map (

 A => A_TB,

 B => B_TB,

 S => S_TB,

 Cout => Cout_TB

);

-- Giriş Vektörlerini Üreten İşlem (Stimulus)

stim_proc: process

begin

 -- Başlangıç (A=0, B=0)

 wait for Clock_Period;

 -- Test 1: A=0, B=1

 B_TB <= '1';

 wait for Clock_Period;

-- Test 2: A=1, B=0

A_TB <= '1';

B_TB <= '0';

wait for Clock_Period;

-- Test 3: A=1, B=1

B_TB <= '1';


wait for Clock_Period;

-- Simülasyonu sonlandır

wait;

end process;

end Behavioral;

 

RCA

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

entity RCA_4BIT_STRUCTURAL is

Port (A : in STD_LOGIC_VECTOR (3 downto 0); -- 4-bit

Giriş A

B : in STD_LOGIC_VECTOR (3 downto 0); -- 4-bit Giriş

B

C_out : out STD_LOGIC_VECTOR (4 downto 0)); -- 5-bit Sonuç (C4 S3 S2 S1 S0)

```
end RCA_4BIT_STRUCTURAL;
```

architecture Structural of RCA_4BIT_STRUCTURAL is

```
-- BİLEŞEN BEYANLARI (HA ve FA'yı kullanacağımızı  
belirtiyoruz)
```

```
component HALF_ADDER
```

```
Port ( A : in STD_LOGIC; B : in STD_LOGIC; S : out  
STD_LOGIC; Cout : out STD_LOGIC);
```

```
end component;
```

```
component FULL_ADDER
```

```
Port ( A : in STD_LOGIC; B : in STD_LOGIC; Cin : in  
STD_LOGIC; S : out STD_LOGIC; Cout : out STD_LOGIC);
```

```
end component;
```

```
-- Elde (Carry) sinyallerini HA/FA'lar arasında taşımak  
için iç sinyal tanımlamaları
```

```
signal C_internal : STD_LOGIC_VECTOR (2 downto 0); --  
C0, C1, C2
```

```
begin
```

```
-- 1. Aşama (Bit 0): Half Adder (HA)
```

```
-- C_out0 --> C_internal(0)
```

```
HA_0: HALF_ADDER
```

```
port map (
```

```
    A => A(0),
```

```
    B => B(0),
```

```
    S => C_out(0),      -- Toplamın 0. biti
```

```
    Cout => C_internal(0) -- C0 (FA1'in Cin'i)
```

```
);
```

```
-- 2. Aşama (Bit 1): Full Adder 1 (FA1)
```

```
-- Cin1 --> C_internal(0), Cout1 --> C_internal(1)
```

```
FA_1: FULL_ADDER
```

```
port map (
```

```

A => A(1),
B => B(1),
Cin => C_internal(0), -- C0
S => C_out(1),        -- Toplamın 1. biti
Cout => C_internal(1) -- C1 (FA2'nin Cin'i)
);

-- 3. Aşama (Bit 2): Full Adder 2 (FA2)
-- Cin2 --> C_internal(1), Cout2 --> C_internal(2)
FA_2: FULL_ADDER
port map (
    A => A(2),
    B => B(2),
    Cin => C_internal(1), -- C1
    S => C_out(2),        -- Toplamın 2. biti
    Cout => C_internal(2) -- C2 (FA3'ün Cin'i)
);

```

-- 4. Aşama (Bit 3): Full Adder 3 (FA3)

-- Cin3 --> C_internal(2), Cout3 --> C_out(4)

FA_3: FULL_ADDDER

port map (

 A => A(3),

 B => B(3),


 Cin => C_internal(2), -- C2

 S => C_out(3), -- Toplamın 3. biti

 Cout => C_out(4) -- C3 (En son elde, 5. bit C4'e
atanır)

);

end Structural;

 

RCA Testbench

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

entity RCA_4BIT_TB is

end RCA_4BIT_TB;

architecture Behavioral of RCA_4BIT_TB is

```

component RCA_4BIT_STRUCTURAL
Port ( A : in STD_LOGIC_VECTOR (3 downto 0);
      B : in STD_LOGIC_VECTOR (3 downto 0);
      C_out : out STD_LOGIC_VECTOR (4 downto 0));
end component;

signal A_TB, B_TB : STD_LOGIC_VECTOR (3 downto 0) :=
(others => '0');
signal C_out_TB : STD_LOGIC_VECTOR (4 downto 0);

constant Delay : time := 100 ns;

begin

  uut: RCA_4BIT_STRUCTURAL
  port map (
    A => A_TB,
    B => B_TB,
    C_out => C_out_TB

```

);

stim_proc: process

begin

-- Test 1: $5 + 3 = 8$ ($0101 + 0011 = 01000$)

A_TB <= "0101";

B_TB <= "0011";

wait for Delay;

-- Test 2: $15 + 1 = 16$ ($1111 + 0001 = 10000$)

A_TB <= "1111";

B_TB <= "0001";

wait for Delay;

-- Test 3: $15 + 15 = 30$ ($1111 + 1111 = 11110$)

A_TB <= "1111";

B_TB <= "1111";

wait for Delay;

```
wait;  
  
end process;  
  
end Behavioral;
```

